

# CMOS Quadrature Front Ends in a single-stage: The LMV Cell

---



**Antonio Liscidini**

[antonio.liscidini@unipv.it](mailto:antonio.liscidini@unipv.it)

Università degli Studi di Pavia, Italy

# Outline

---


- **The LNA-Mixer-VCO cell**
  - The LC tank Oscillator as a Mixer
  - Single/Double Switching Pair SOM
  - LNA introduction
- **Loss Mechanisms in the SOM**
  - Output parasitic capacitances
  - Common Mode and Differential losses
  - Voltage Mode vs. Current Mode
- **I & Q LMV Cells**
  - Quadrature at the VCO
  - Quadrature at the RF signal path
- **Prototypes**
  - GPS RF Front-End
  - ZigBee Receiver
- **Conclusions**

# Outline

---

- **The LNA-Mixer-VCO cell**
  - The LC tank Oscillator as a Mixer
  - Single/Double Switching Pair SOM
  - LNA introduction
- **Loss Mechanisms in the SOM**
  - Output parasitic capacitances
  - Common Mode and Differential losses
  - Voltage Mode vs. Current Mode
- **I & Q LMV Cells**
  - Quadrature at the VCO
  - Quadrature at the RF signal path
- **Prototypes**
  - GPS RF Front-End
  - ZigBee Receiver
- **Conclusions**


# Mixer inside LC Oscillator

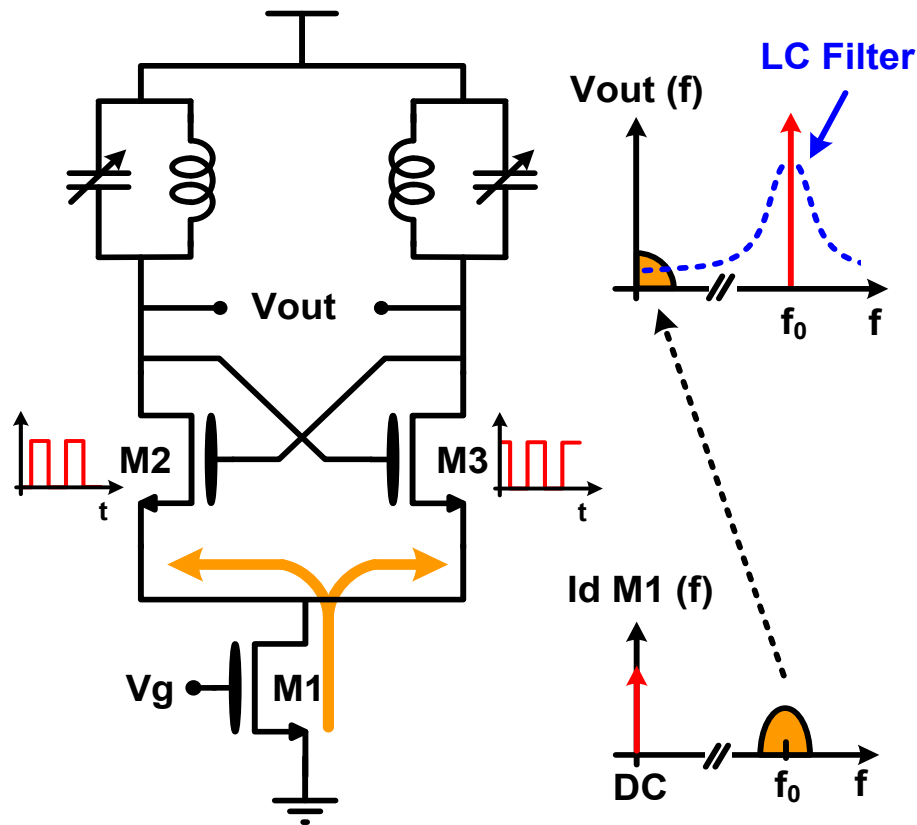

- Any RF signal in the VCO bias current is naturally down-converted at IF
- LC tank attenuates the low frequency components of  $V_{out}$

**Problem: how to sense the down-converted current signal preserving oscillation**

# Basic Idea: Bias Splitting

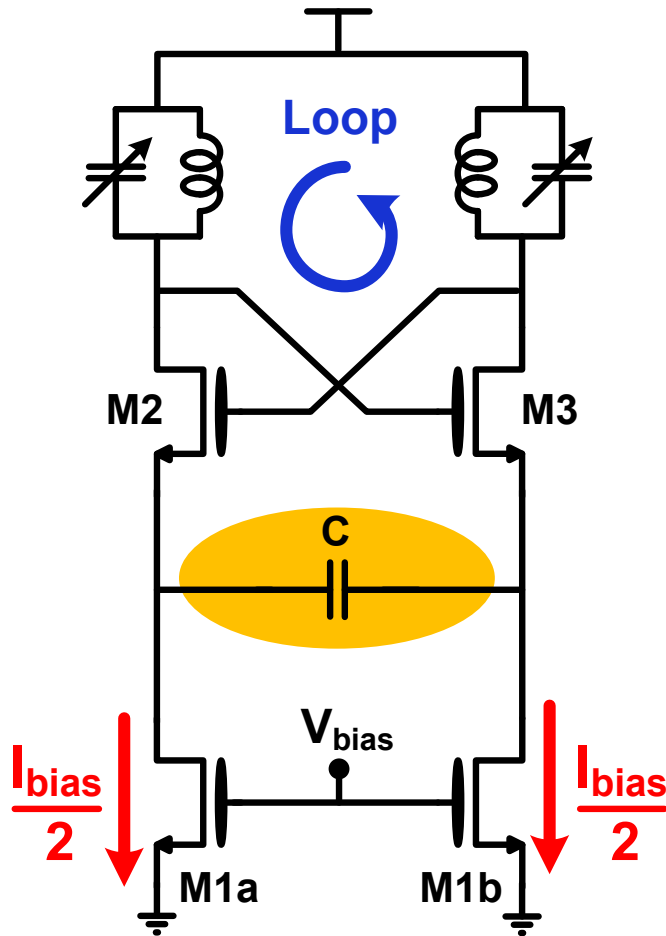


- M1 is spitted in two transistors and a capacitor  $C$  is used to close the loop at RF
- $C$  is a degeneration for M2 and M3


$$\omega_{LO}C \gg gm_{2,3}$$

- At low frequency it has an high impedance between M2,M3 sources.


# Bias Splitting SOM

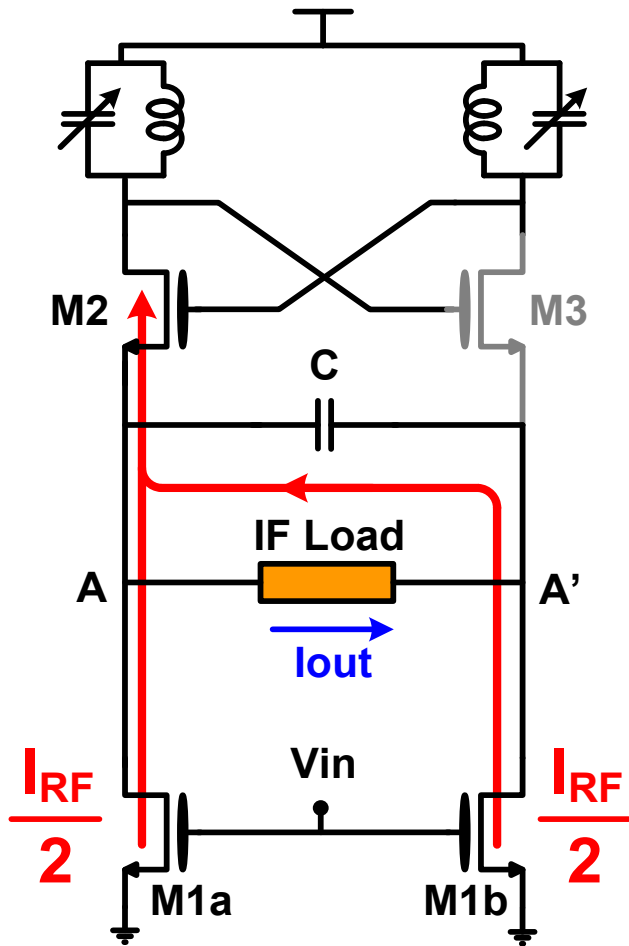



Semi-period with M2 on

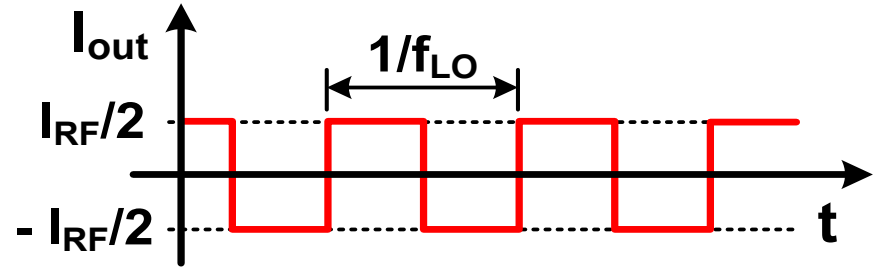

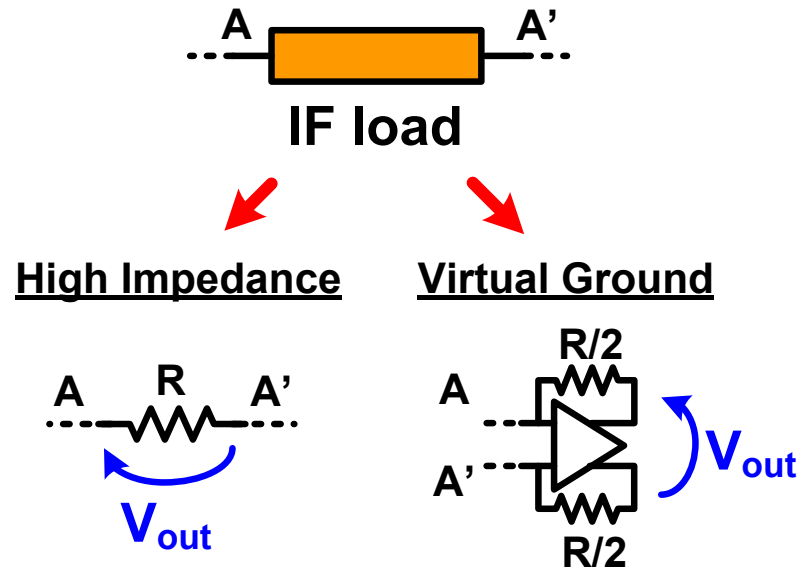- Only half of the signal current flows through IF load



# Double Switching Pairs

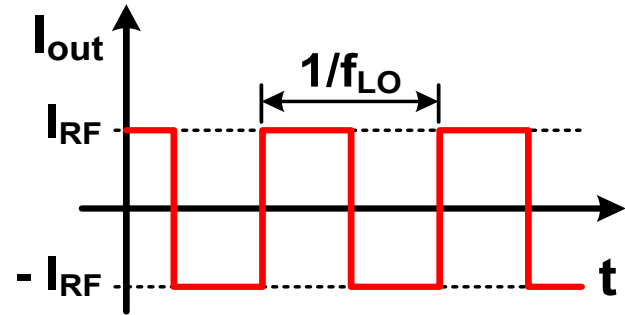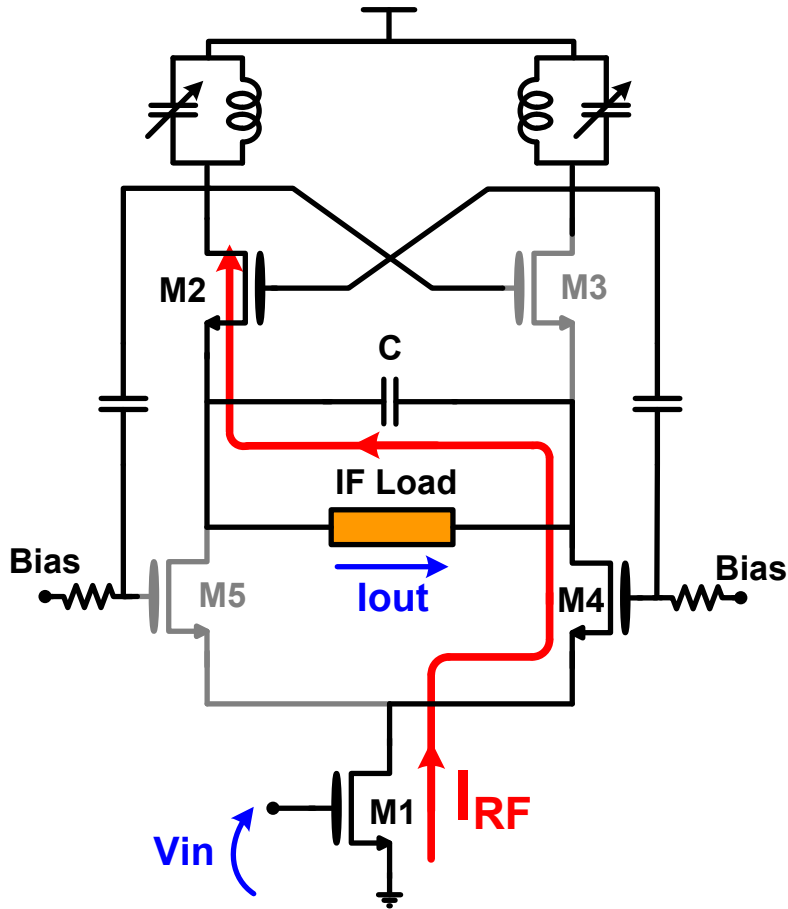


- All RF signal current is down converted leading:

$$\frac{I_{out}}{V_{in}} = \frac{2}{\pi} g_{m1}$$

Semi-period with M2 and M4 on

# LNA-Mixer-VCO (LMV) Cell

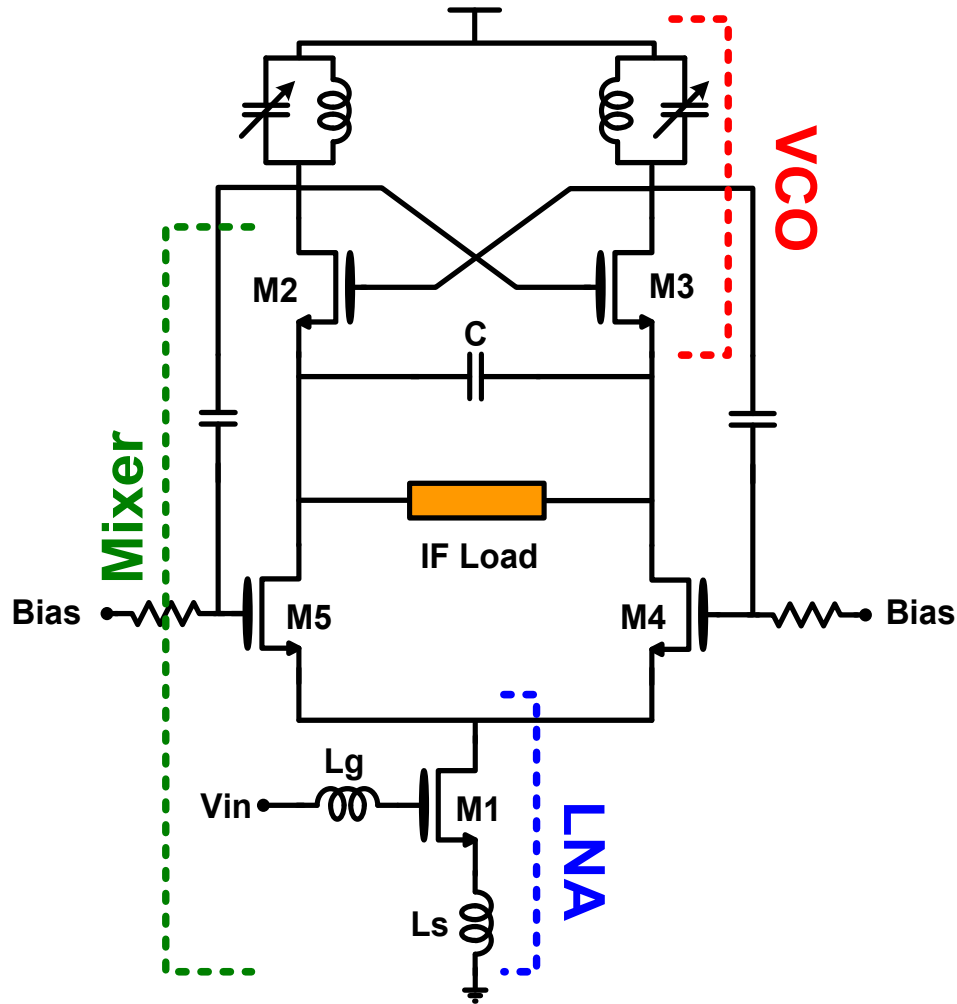

- LNA is implemented re-using M1 in a inductive degenerated topology.
- Three transistor stacked but minimum  $V_{DD}$  is  $1 V_{TH}$  plus  $3 V_{OV}$

**LNA, Mixer and VCO  
share bias and devices**


# Outline

---

- **The LNA-Mixer-VCO cell**
  - The LC tank Oscillator as a Mixer
  - Single/Double Switching Pair SOM
  - LNA introduction
- **Loss Mechanisms in the SOM**
  - Output parasitic capacitances
  - Common Mode and Differential losses
  - Voltage Mode vs. Current Mode
- **I & Q LMV Cells**
  - Quadrature at the VCO
  - Quadrature at the RF signal path
- **Prototypes**
  - GPS RF Front-End
  - ZigBee Receiver
- **Conclusions**


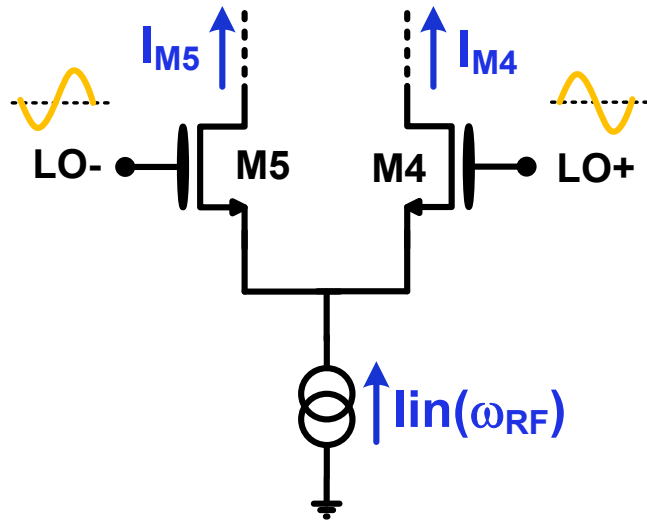
# Differential and Common Mode Components (1)




- The current injected by the first switching pair has two components:
  - A **Common Mode** not down converted
  - A **Differential** mixed at  $\omega_{RF}-\omega_{LO}$

$$\begin{cases}
 I_{M4} = \frac{I_{in}}{2} (1 + \text{sign}[\cos(\omega_{LO}t)]) = \underbrace{\frac{I_{in}(\omega_{RF})}{2}}_{\text{Common Mode}} + \underbrace{\frac{I_{in}(\omega_{RF}-\omega_{LO})}{\pi}}_{\text{Differential Part}} + \dots \\
 I_{M5} = \frac{I_{in}}{2} (1 - \text{sign}[\cos(\omega_{LO}t)]) = \frac{I_{in}(\omega_{RF})}{2} - \frac{I_{in}(\omega_{RF}-\omega_{LO})}{\pi} + \dots
 \end{cases}$$


# Differential and Common Mode Components (2)

The *double switching pair SOM* can be transform in “the sum” of two *bias splitting SOM*



Common Mode RF Component

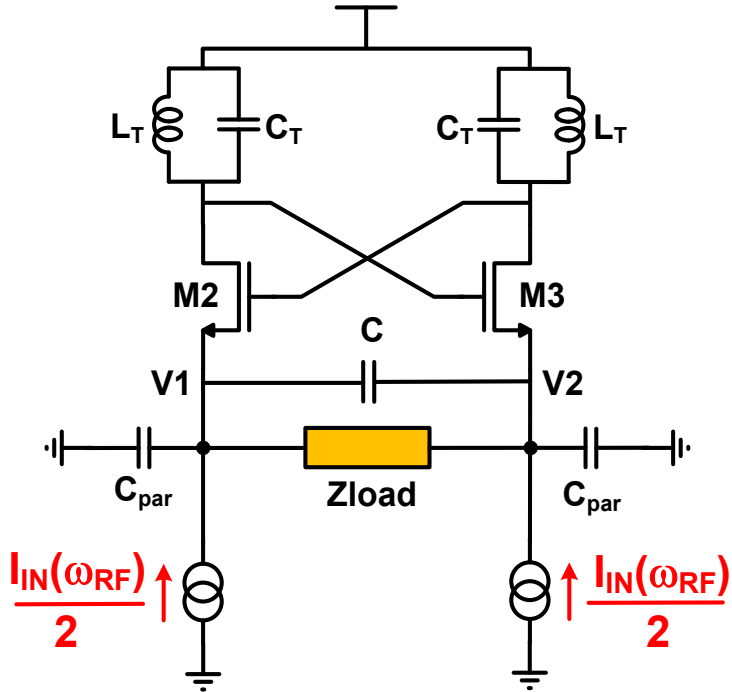

Differential IF Components

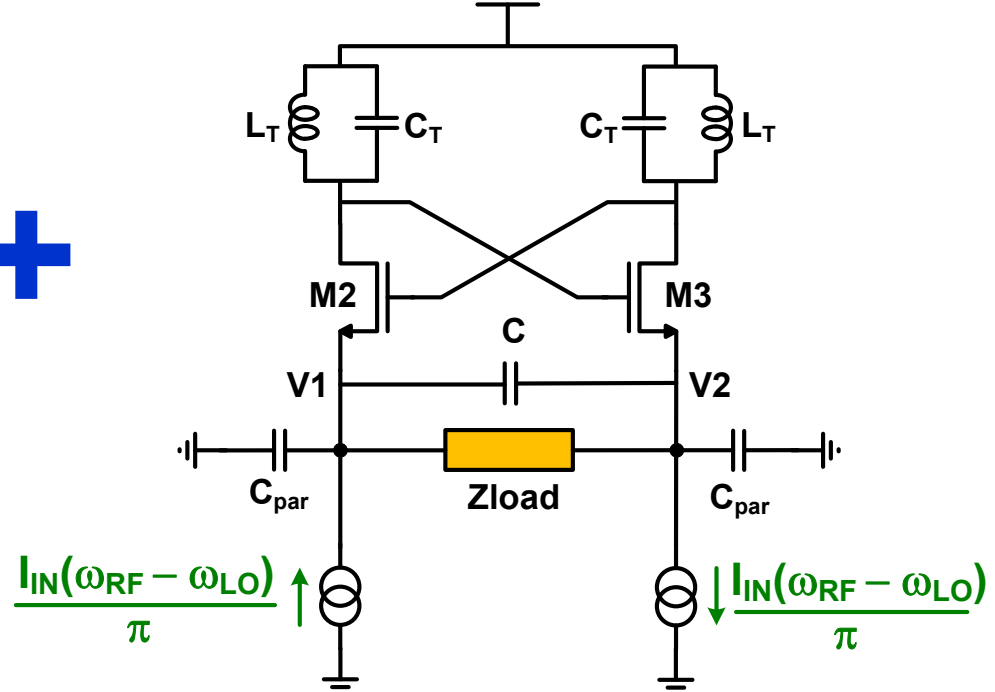
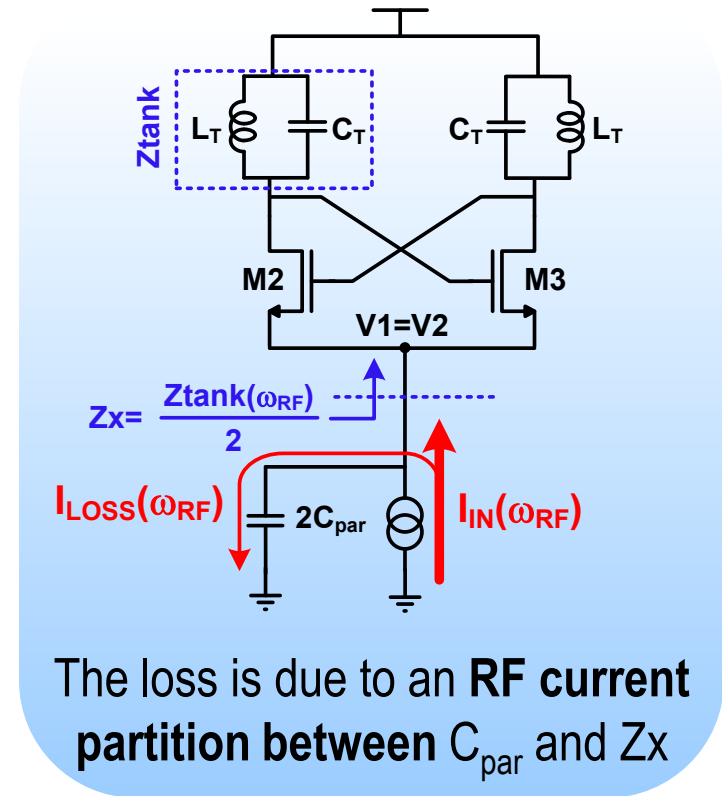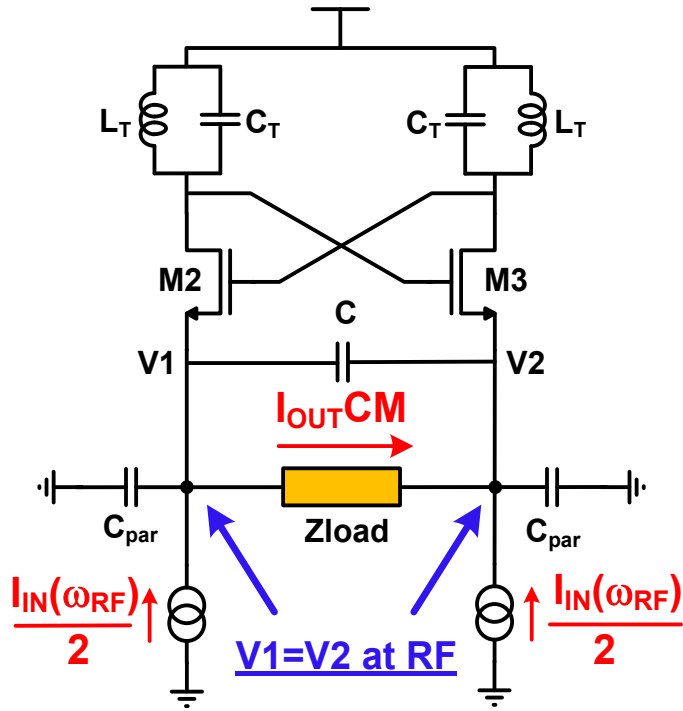
# Losses at RF Frequency (Common Mode Components)




Current and Voltage Mode LMV has the same **Common Mode conversion gain**

$$I_{OUT\ CM}(\omega_{RF} - \omega_{LO}) = \frac{1}{\pi} \frac{1}{1 + j\omega_{RF} C_{par} \cdot Z_{tank}(\omega_{RF})} I_{IN}(\omega_{RF})$$
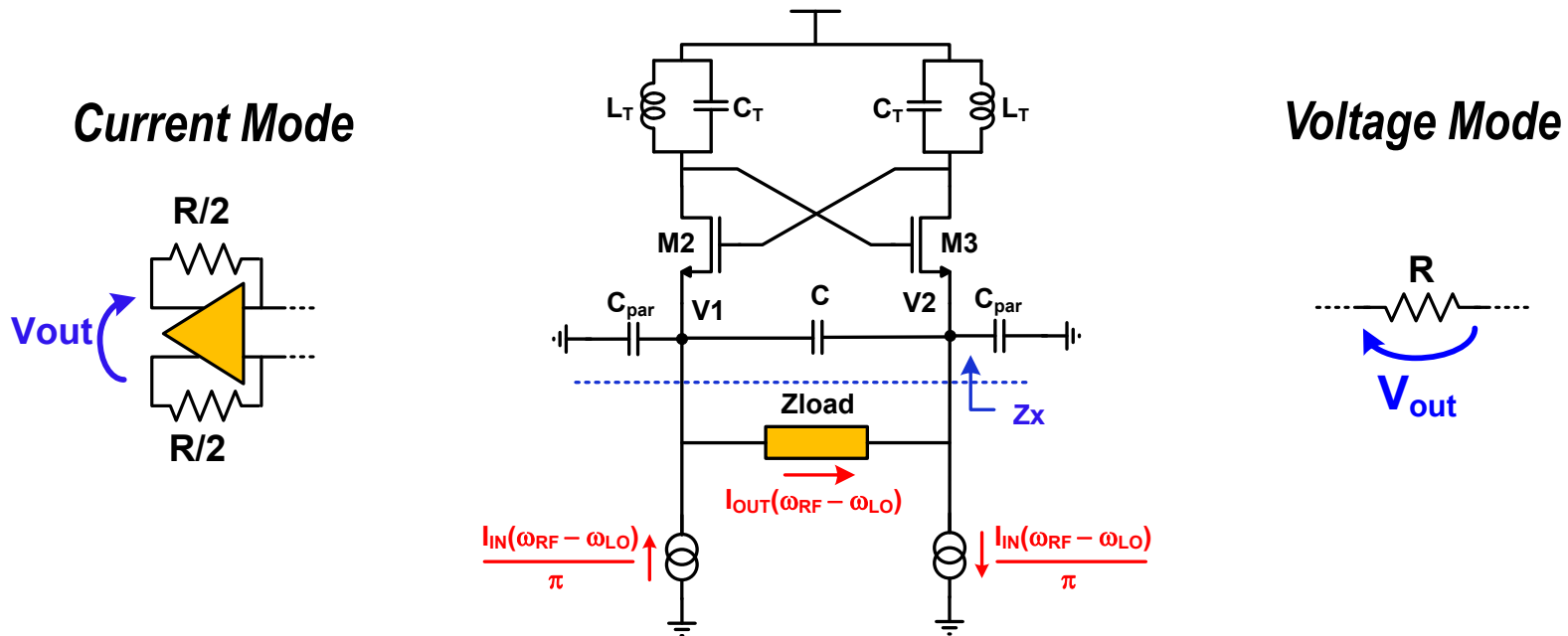
# Losses at IF Frequency (Differential Components)

The IF losses depend on a current partition between IF load and  $Z_x$



- $Z_{load} \approx 0 \rightarrow$  No losses


$$I_{OUT}^{DIFF}(\omega_{RF} - \omega_{LO}) = \frac{1}{\pi} I_{IN}(\omega_{RF})$$

- Non linear, time variant current partition with  $Z_x$

**Current Mode has no losses for the differential components**
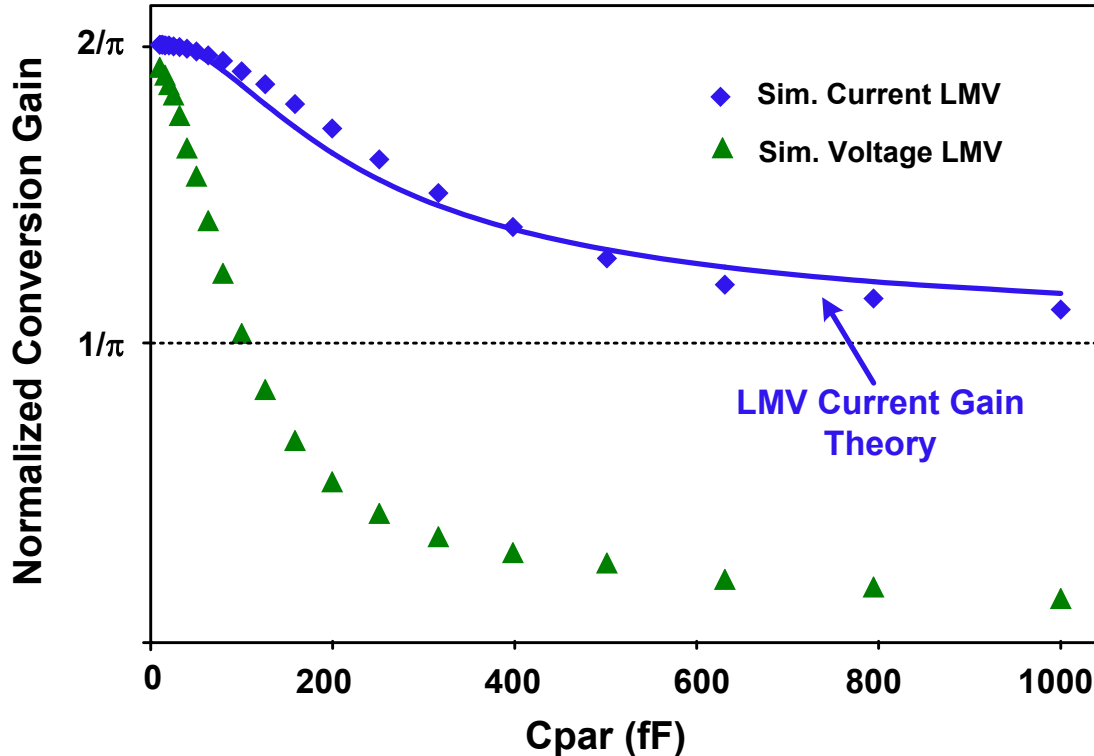
# Voltage Mode vs. Current Mode

The total down-converted signal is given by  $I_{OUT}^{CM} + I_{OUT}^{DIFF}$



Current mode Gain

$$I_{OUT}(\omega_{RF} - \omega_{LO}) = \frac{1}{\pi} \frac{2 + j\omega_{RF} C_{par} \cdot Z_{tank}(\omega_{RF})}{1 + j\omega_{RF} C_{par} \cdot Z_{tank}(\omega_{RF})} I_{IN}(\omega_{RF})$$


# Outline

---


- **The LNA-Mixer-VCO cell**
  - The LC tank Oscillator as a Mixer
  - Single/Double Switching Pair SOM
  - LNA introduction
- **Loss Mechanisms in the SOM**
  - Output parasitic capacitances
  - Common Mode and Differential losses
  - Voltage Mode vs. Current Mode
- **I & Q LMV Cells**
  - Quadrature at the VCO
  - Quadrature at the RF signal path
- **Prototypes**
  - GPS RF Front-End
  - ZigBee Receiver
- **Conclusions**

# Quadrature Receivers

## Quadrature at LO

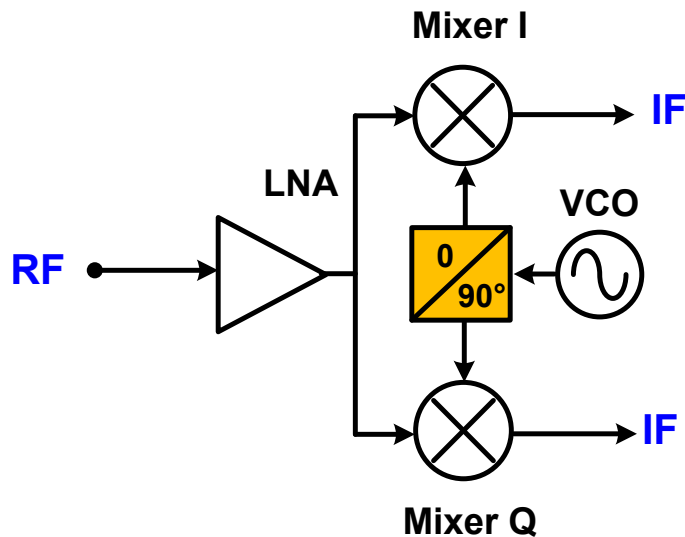

## Quadrature on RF signal path

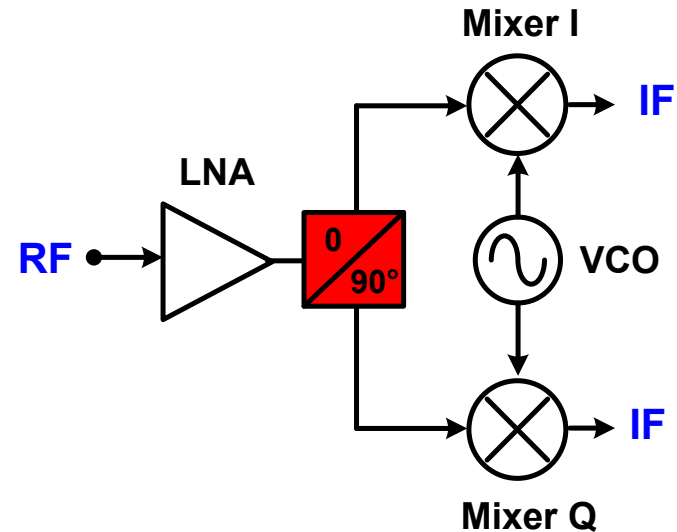


- Good quadrature accuracy
- Several architectures available:  
(*Quadrature VCOs, Divider, Polyphase Filter*)

- Only two phase for LO signal
- Losses on RF path



# Cross Coupled LMV Quadrature (2)

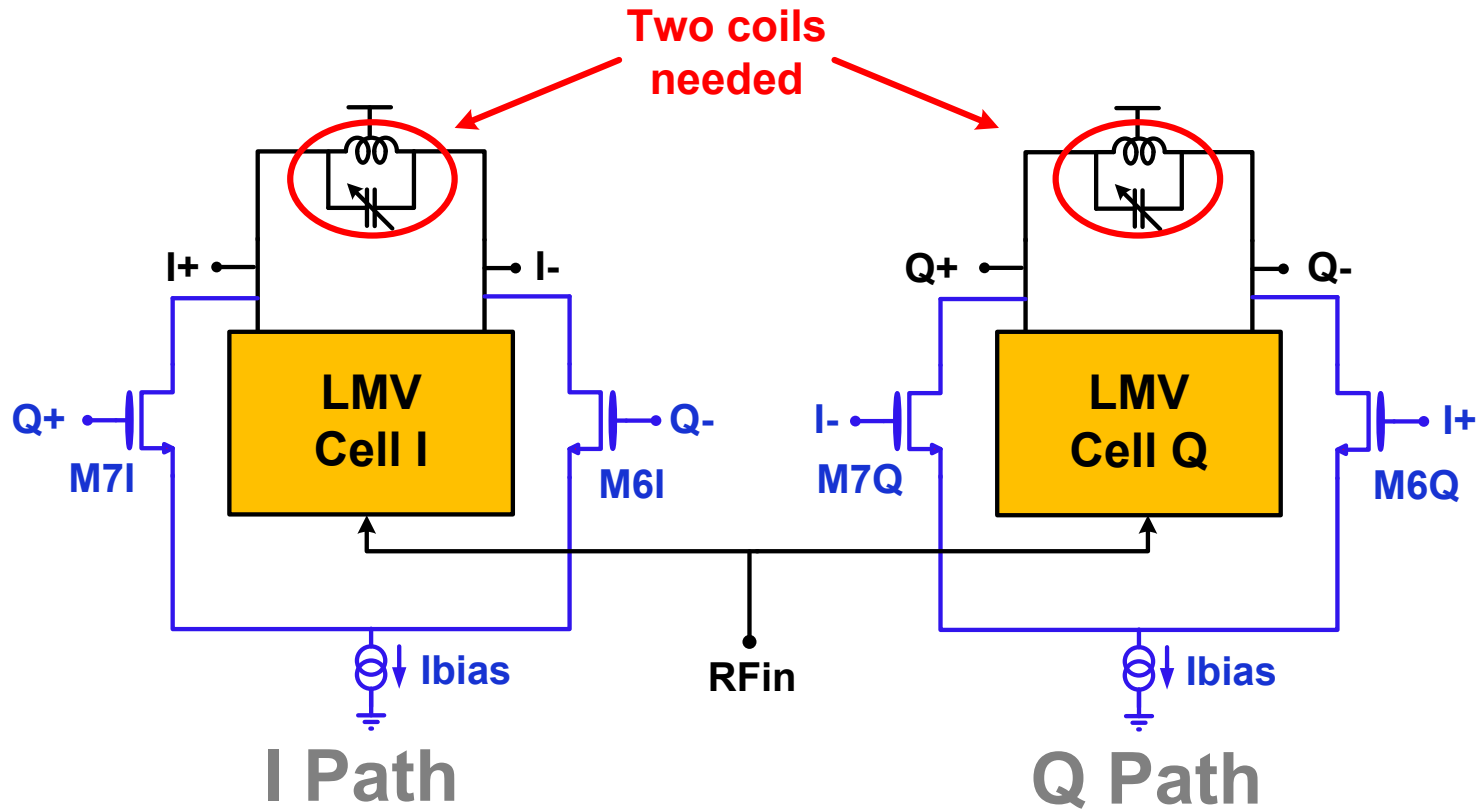

- Good quadrature accuracy
- **Two LMV Cells** (Double area and power)

How to reduce number of inductors?


# Quadrature LMV Tank Sharing

- Share the tank between the two LMV and provide quadrature on RF path




I & Q bias in the same tank:  
dissipation and area reduced

How to realize a quadrature LNA?

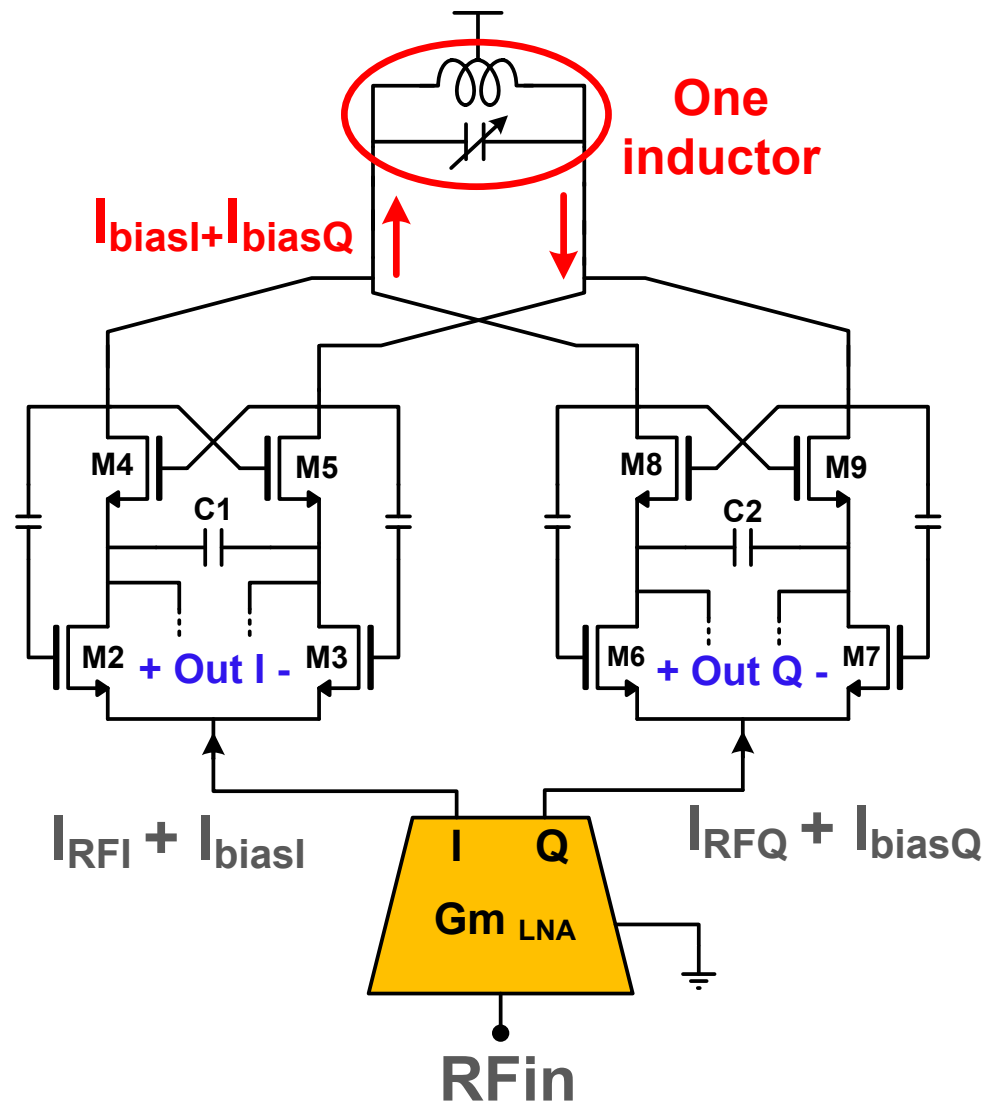


# LNA Quadrature Generation

To the Mixers

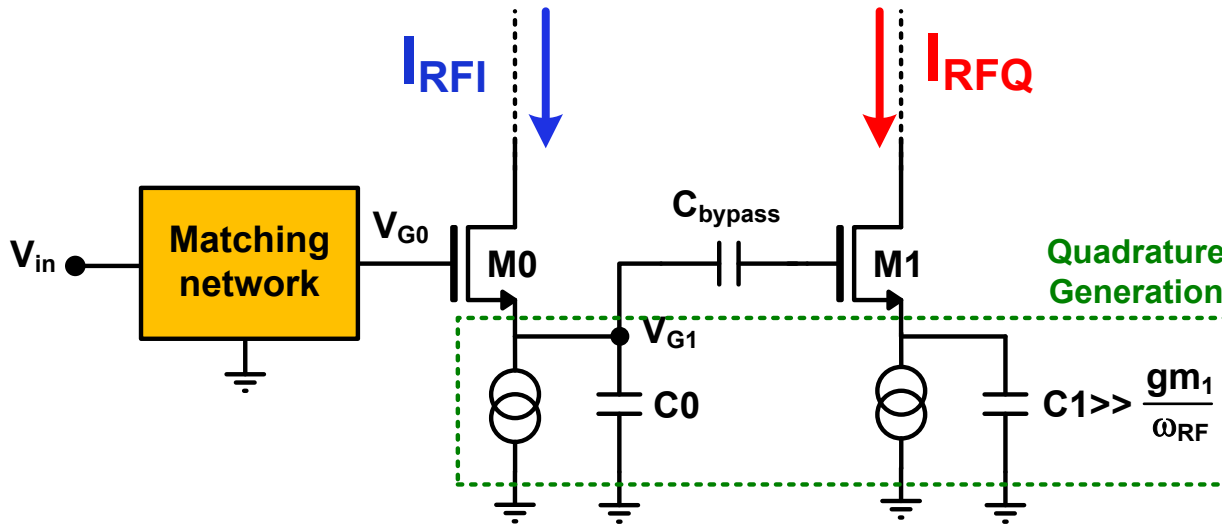

$$I_{RFI} = \frac{j\omega C_0}{1 + j\omega C_0/gm_0} V_{in}$$
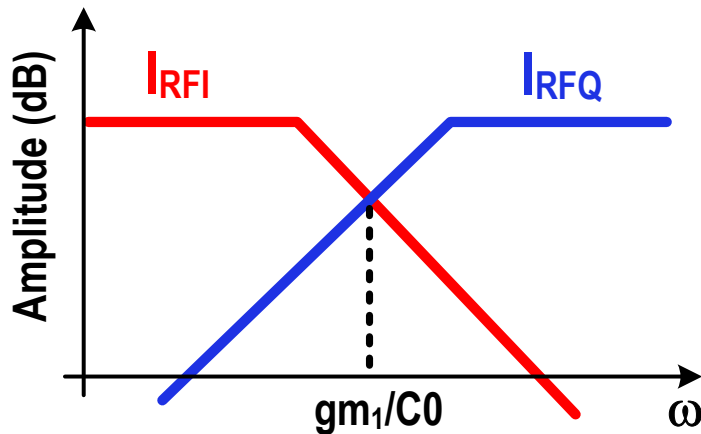
$$I_{RFQ} = \frac{gm_1}{j\omega C_0} I_{RFI}$$





- Signal **quadrature** guaranteed on a **wide range**
- **Amplitude match** obtained only close to  $gm_1/C_0$

# LNA matching network

- $Z_{in} = \frac{R}{1 + Q^2}$

- $Q = \omega_0 RC$

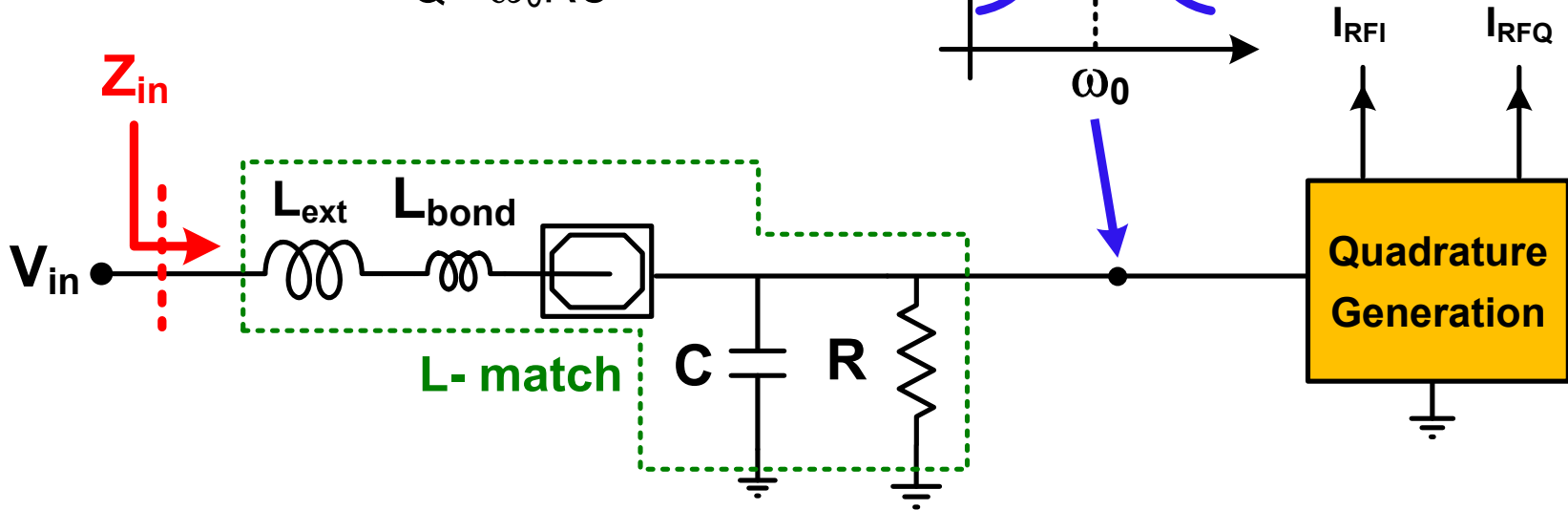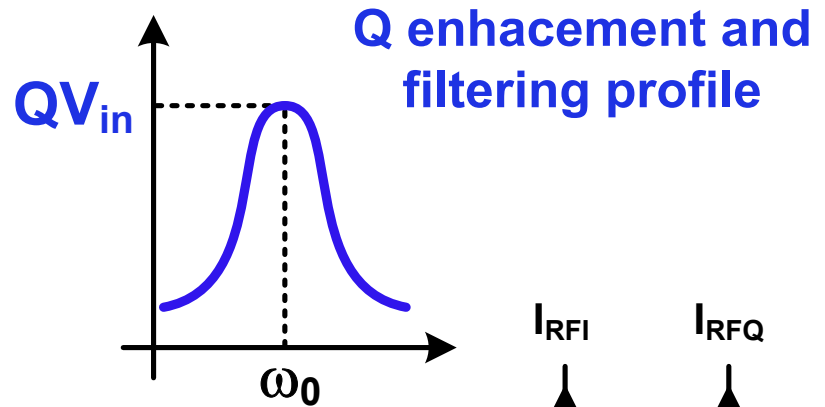


The **L-match network** provides a **filtering action** for out of band blockers and a **gain boost** to reduce noise

# Outline

---

- **The LNA-Mixer-VCO cell**
  - The LC tank Oscillator as a Mixer
  - Single/Double Switching Pair SOM
  - LNA introduction
- **Loss Mechanisms in the SOM**
  - Output parasitic capacitances
  - Common Mode and Differential losses
  - Voltage Mode vs. Current Mode
- **I & Q LMV Cells**
  - Quadrature at the VCO
  - Quadrature at the RF signal path
- **Prototypes**
  - GPS RF Front-End
  - ZigBee Receiver
- **Conclusions**


# Low IF Receiver with Quadrature @ LO

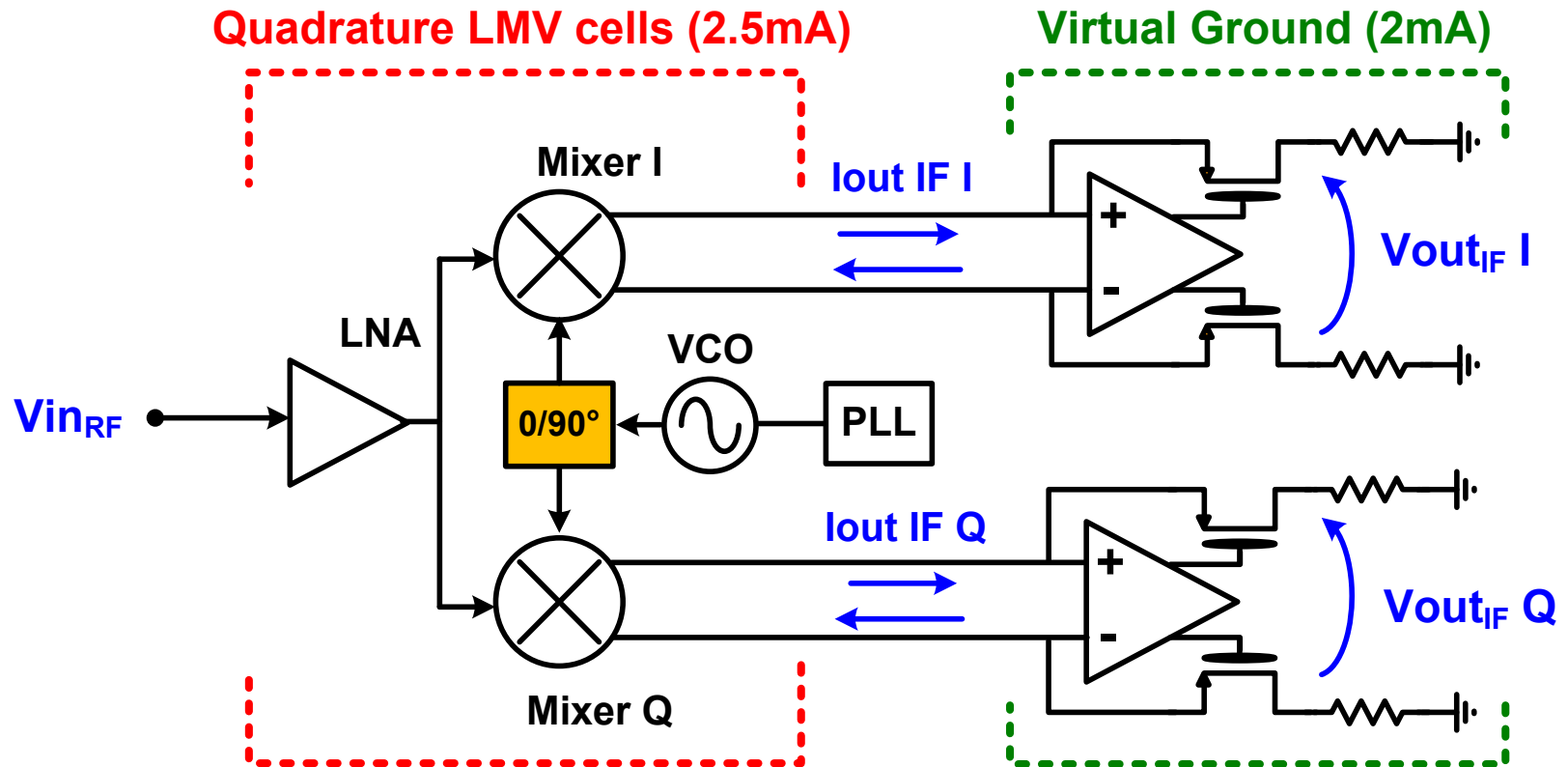

GPS quadrature Front-End: Low IF architecture at 4MHz

[Liscidini et al. ISSCC'06]


# Chip Micrograph

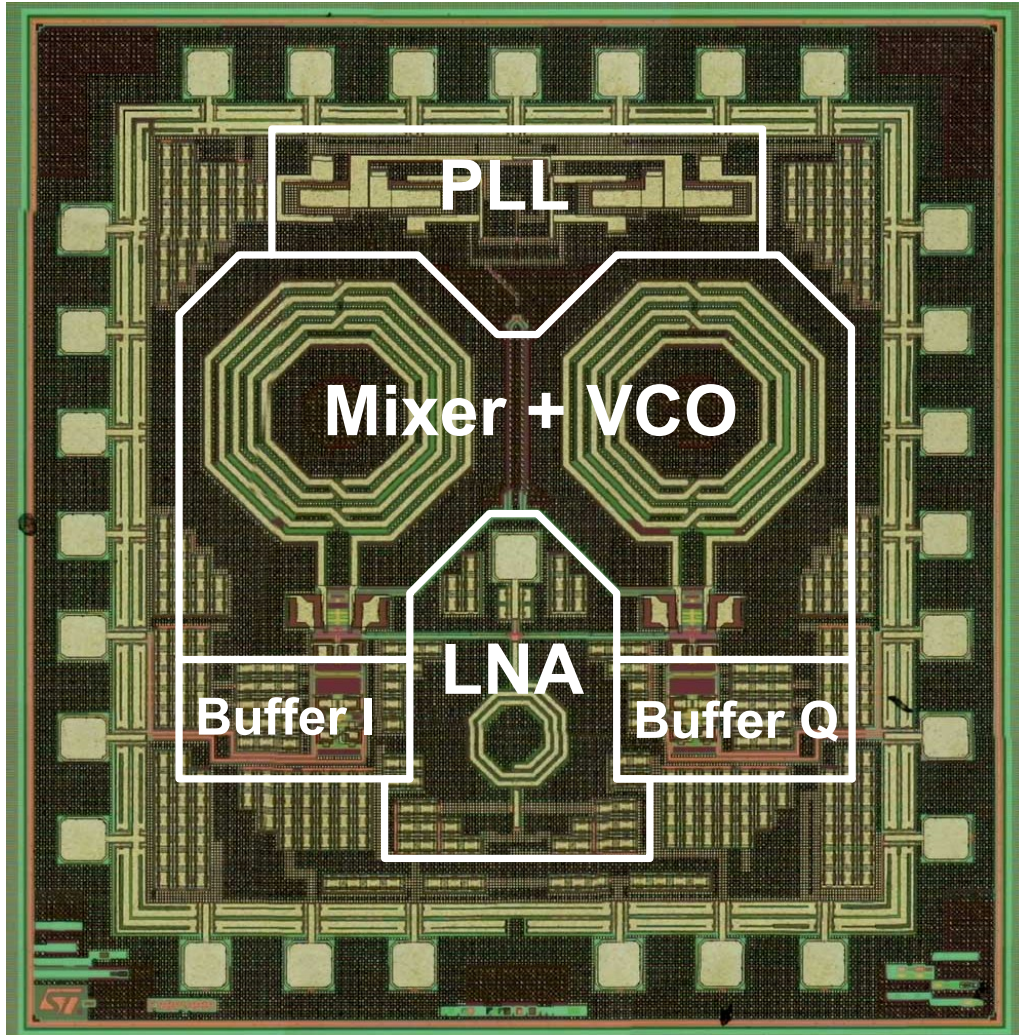


- Active area only 1.5 mm<sup>2</sup>
- Differential inductors for VCO tanks
- PAD ESD protected
- Technology CMOS 0.13 μm

# Input Matching and Gain

## Input Matching

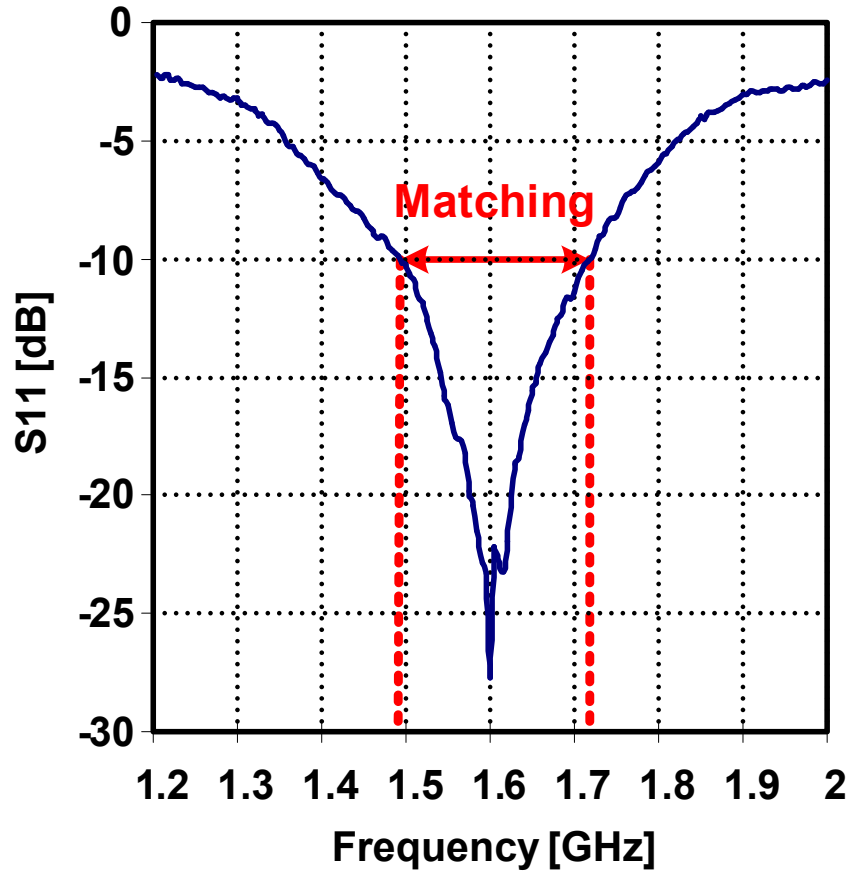


## Output Gain

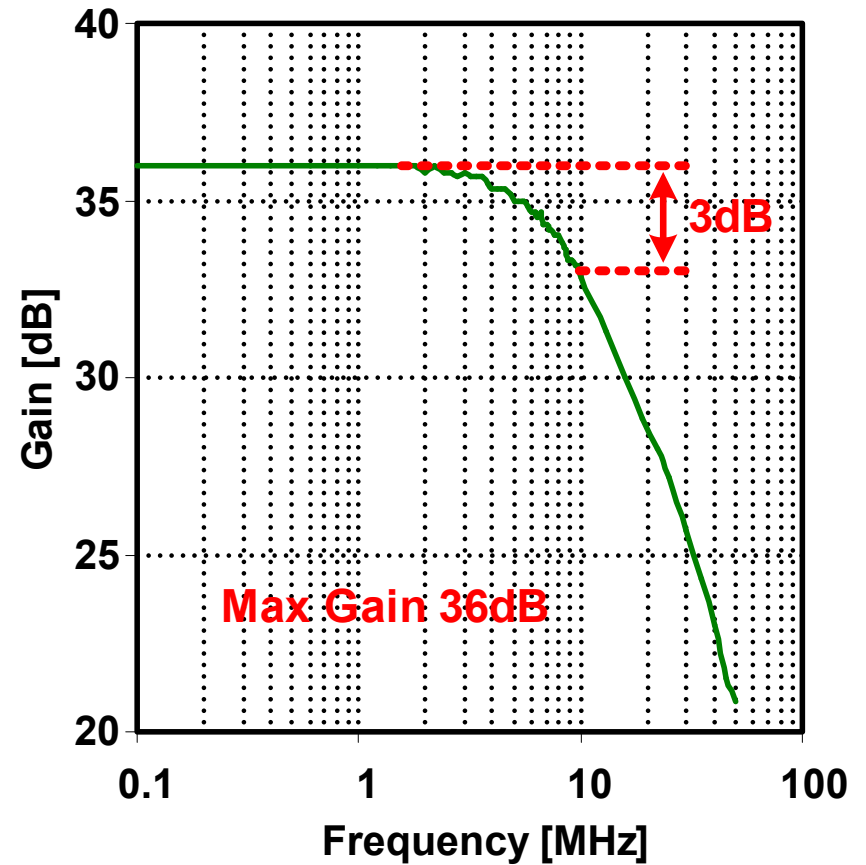


# NF and VCO Phase Noise

## Noise Figure

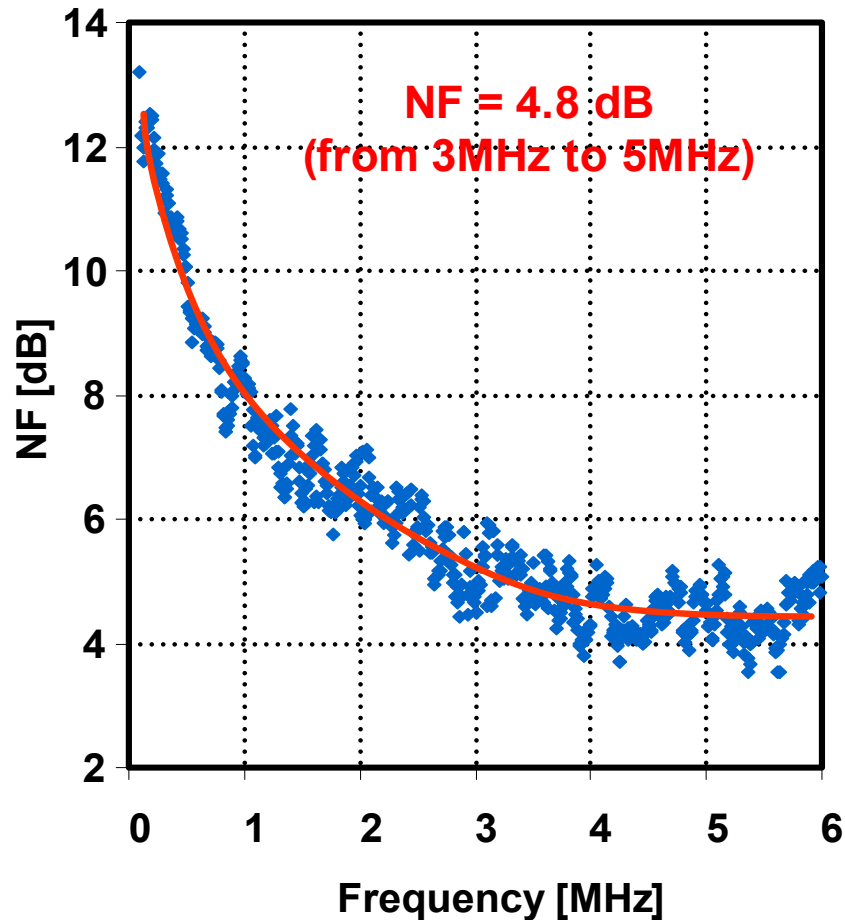

## Phase Noise

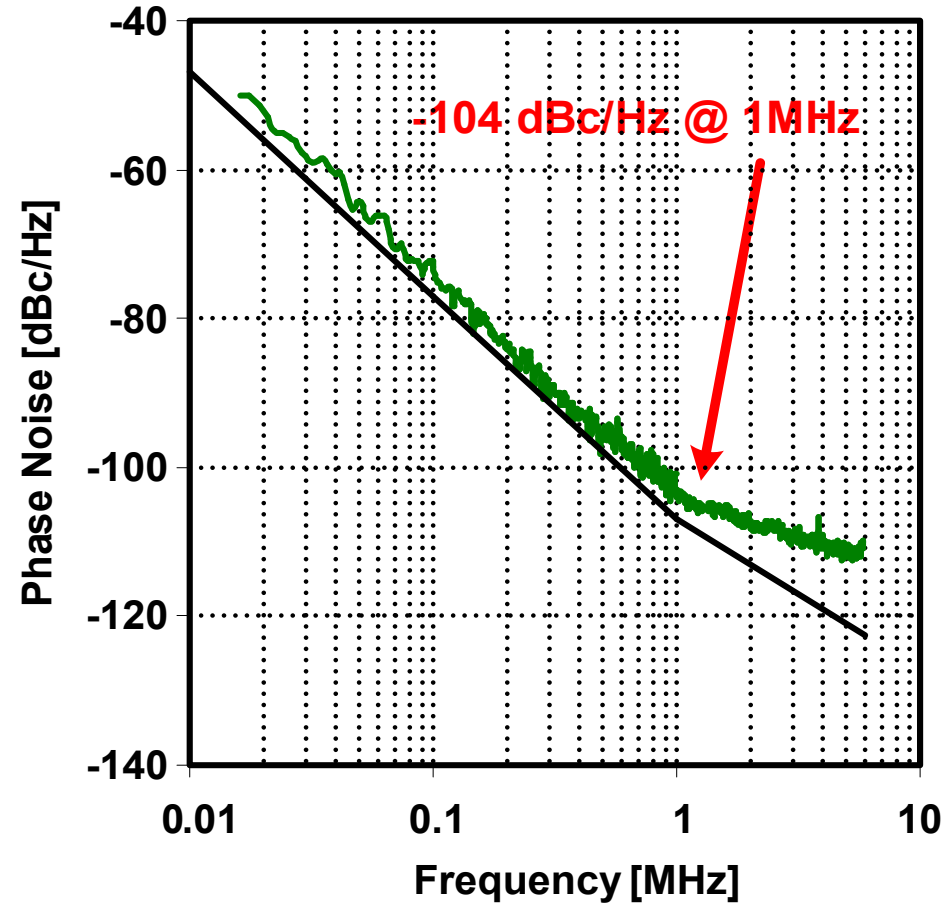

# The State of Art

	[1]	[2]	[3]	This Work
Gain	(25)+60 dB	(50)+80 dB	(33)+60 dB	36dB
NF	4dB	4dB	8.5dB	4.8dB
IIP3	n.a.	-15dBm	n.a.	-19dBm
1dB Comp. Point	-28dBm	n.a.	n.a.	-31dBm
PN @ 1MHz	-95dBc/Hz	-107dBc/Hz	-109dBc/Hz	-104dBc/Hz
LO leak. at input	-66dBm	n.a.	n.a.	-55dBm
<b>Total Power</b>	<b>35mW</b>	<b>27mW</b>	<b>19 mW</b>	<b>11mW*</b>

[1] G. Montagna *et al.* JSSC, July 2003 (CMOS 018  $\mu\text{m}$ )

[2] F. Behbahani *et al.* JSSC, Dec. 2002 (CMOS 0.35  $\mu\text{m}$ )

[3] J. Ko *et al.* JSSC, July 2005 (CMOS 0.18  $\mu\text{m}$ )


**\* Included PLL (4.6 mW)**

# Outline

---

- **The LNA-Mixer-VCO cell**
  - The LC tank Oscillator as a Mixer
  - Single/Double Switching Pair SOM
  - LNA introduction
- **Loss Mechanisms in the SOM**
  - Output parasitic capacitances
  - Common Mode and Differential losses
  - Voltage Mode vs. Current Mode
- **I & Q LMV Cells**
  - Quadrature at the VCO
  - Quadrature at the RF signal path
- **Prototypes**
  - GPS RF Front-End
  - ZigBee Receiver
- **Conclusions**
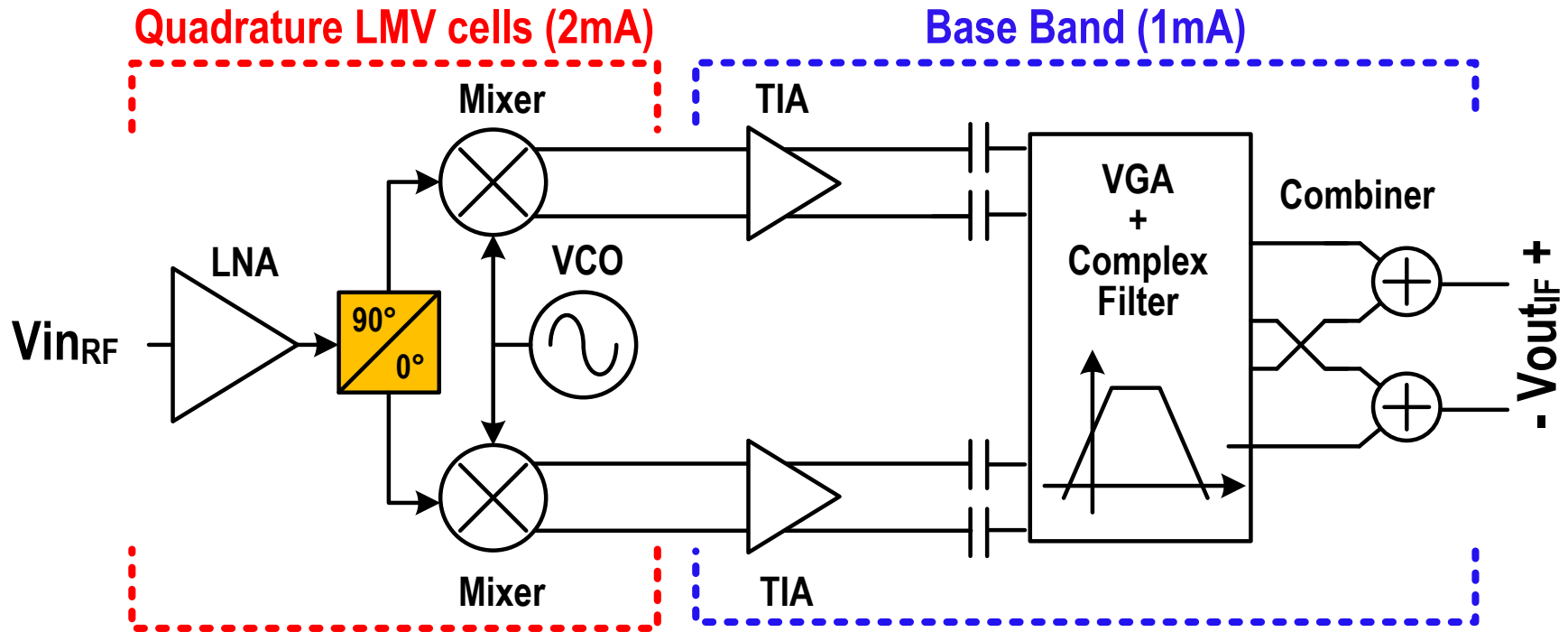
# Low IF Receiver with Quadrature on RF path




ZigBee Quadrature Receiver: Low IF architecture at 2MHz

[Liscidini et al. ISSCC'08]


# gmC Complex Filter

## 3<sup>rd</sup> Order Real Butterworth

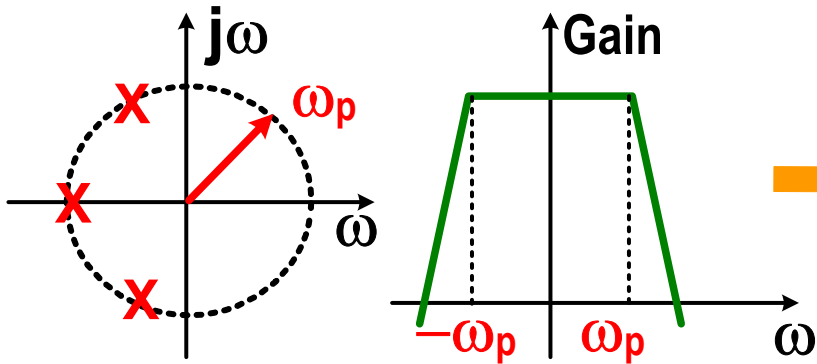

Real Pole= $\omega_p$
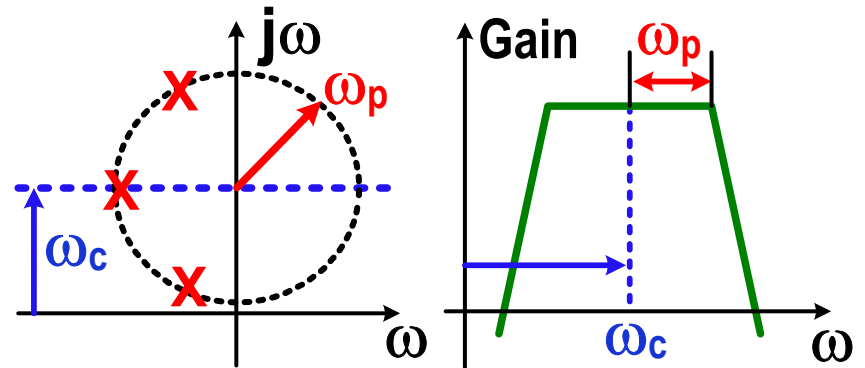
## 3<sup>rd</sup> Order Complex Butterworth




Complex Pole= $\omega_p + j\omega_c$

From a real to a complex filter there is a **shift of frequencies**:

$$j\omega \rightarrow j(\omega - \omega_c)$$

The  $f_c$  shift is the center frequency of the new band-pass


# gmC Complex pole Synthesis

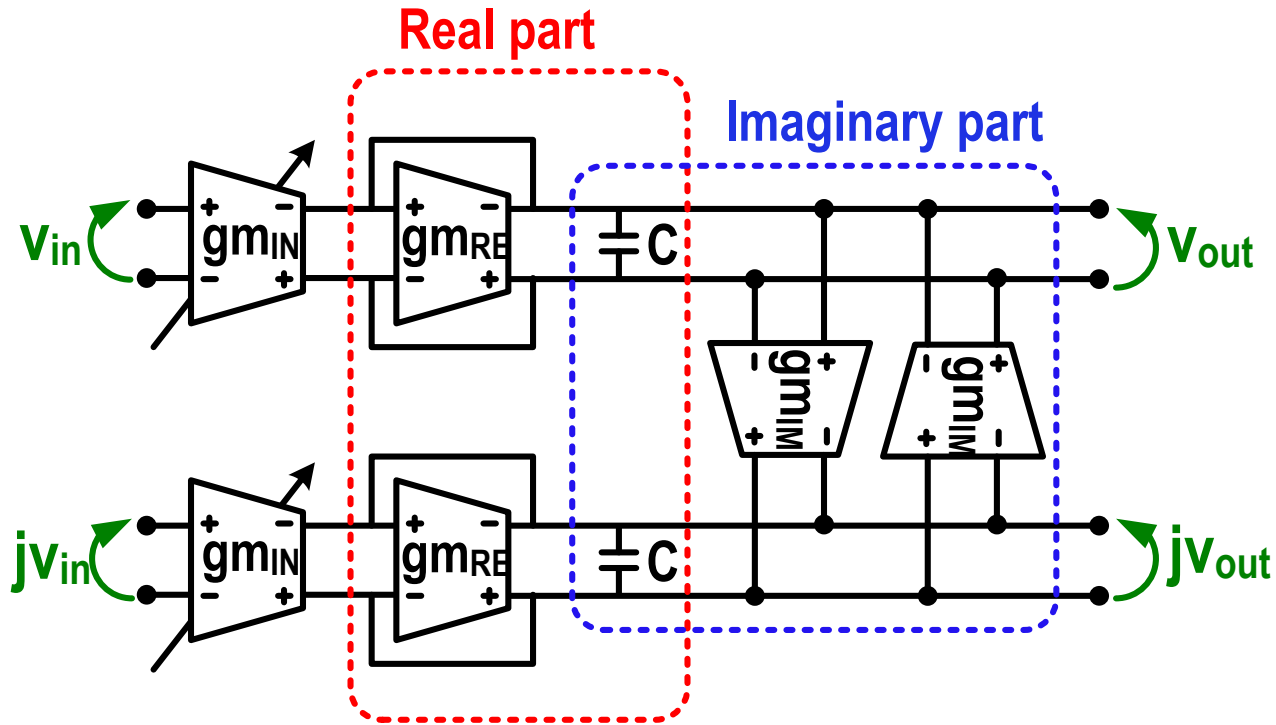

Complex pole realized as  $\omega_{\text{comp}} = \frac{gm_{\text{RE}}}{2C} + j \frac{gm_{\text{IM}}}{2C}$

Gain stage and pole frequency controlled by gm


# Chip Micrograph

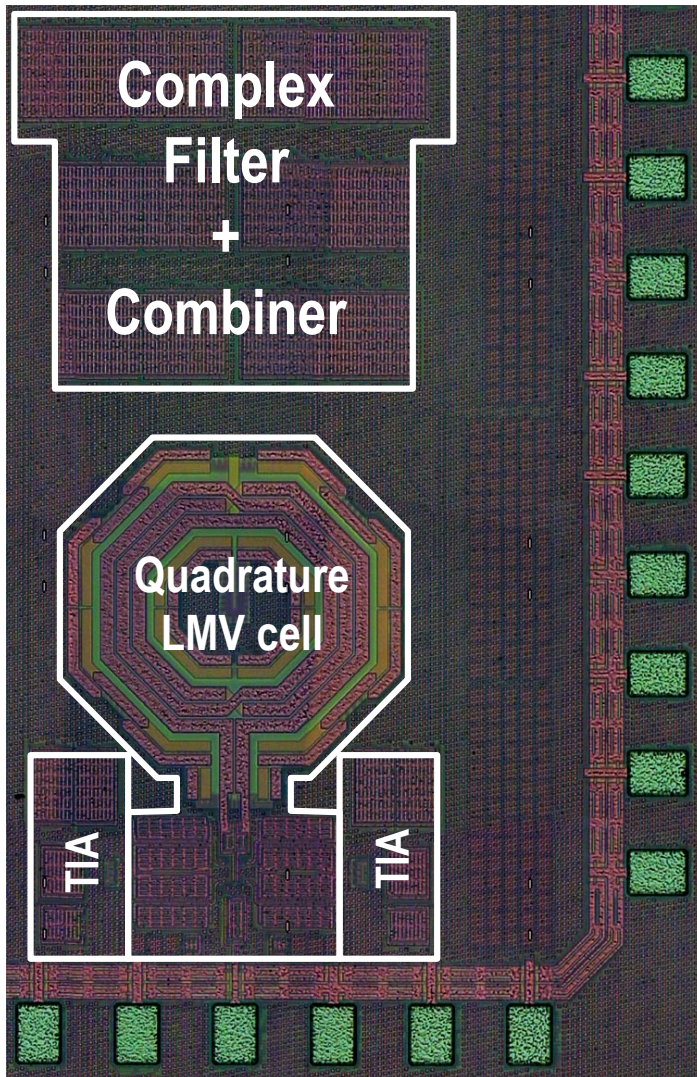


- Technology CMOS 90 nm
- Only one integrated inductor
- Active area only  $0.35 \text{ mm}^2$   
(RF section area similar to BB section area)

# Input Matching

---

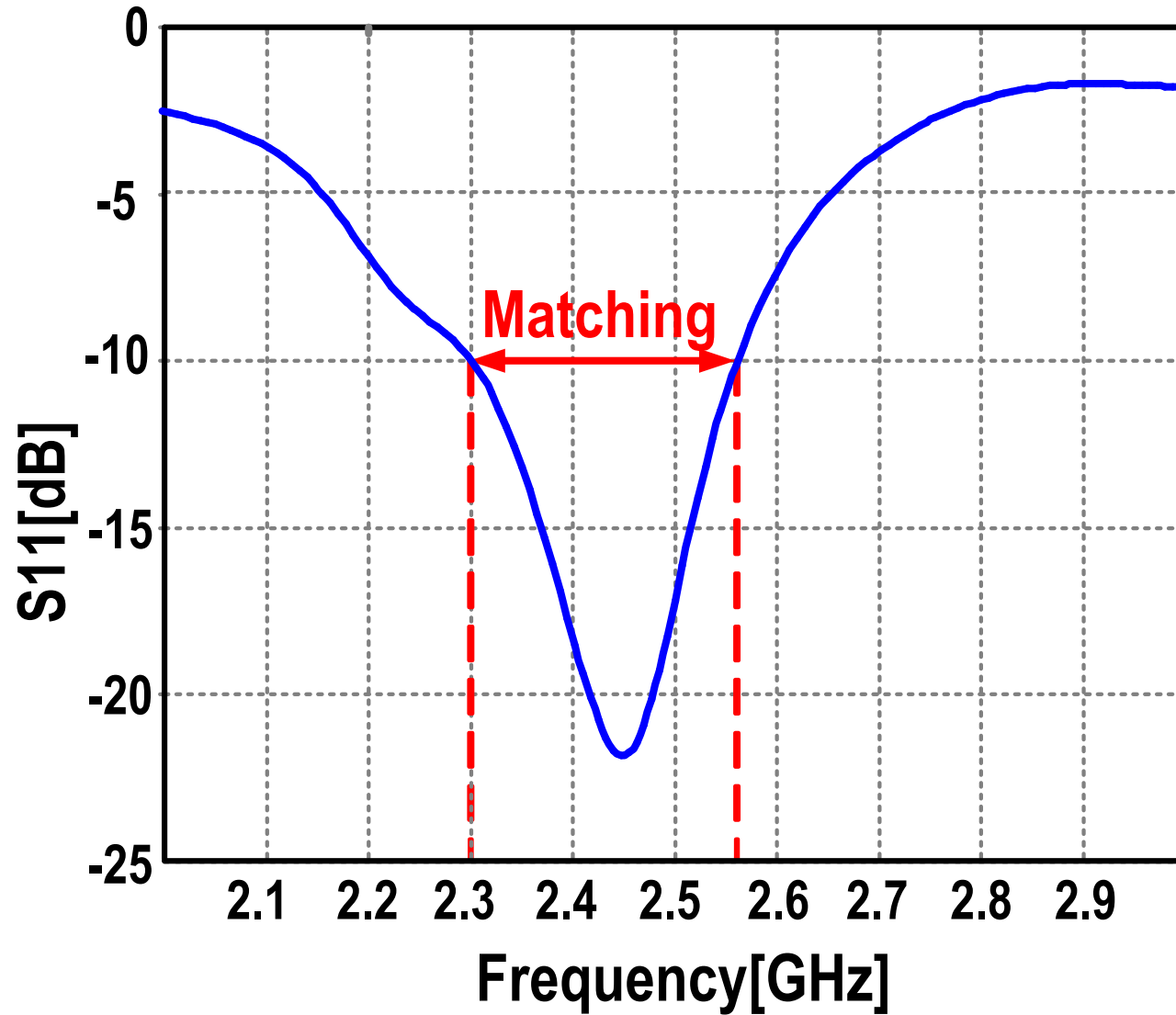

# IF Gain Profile

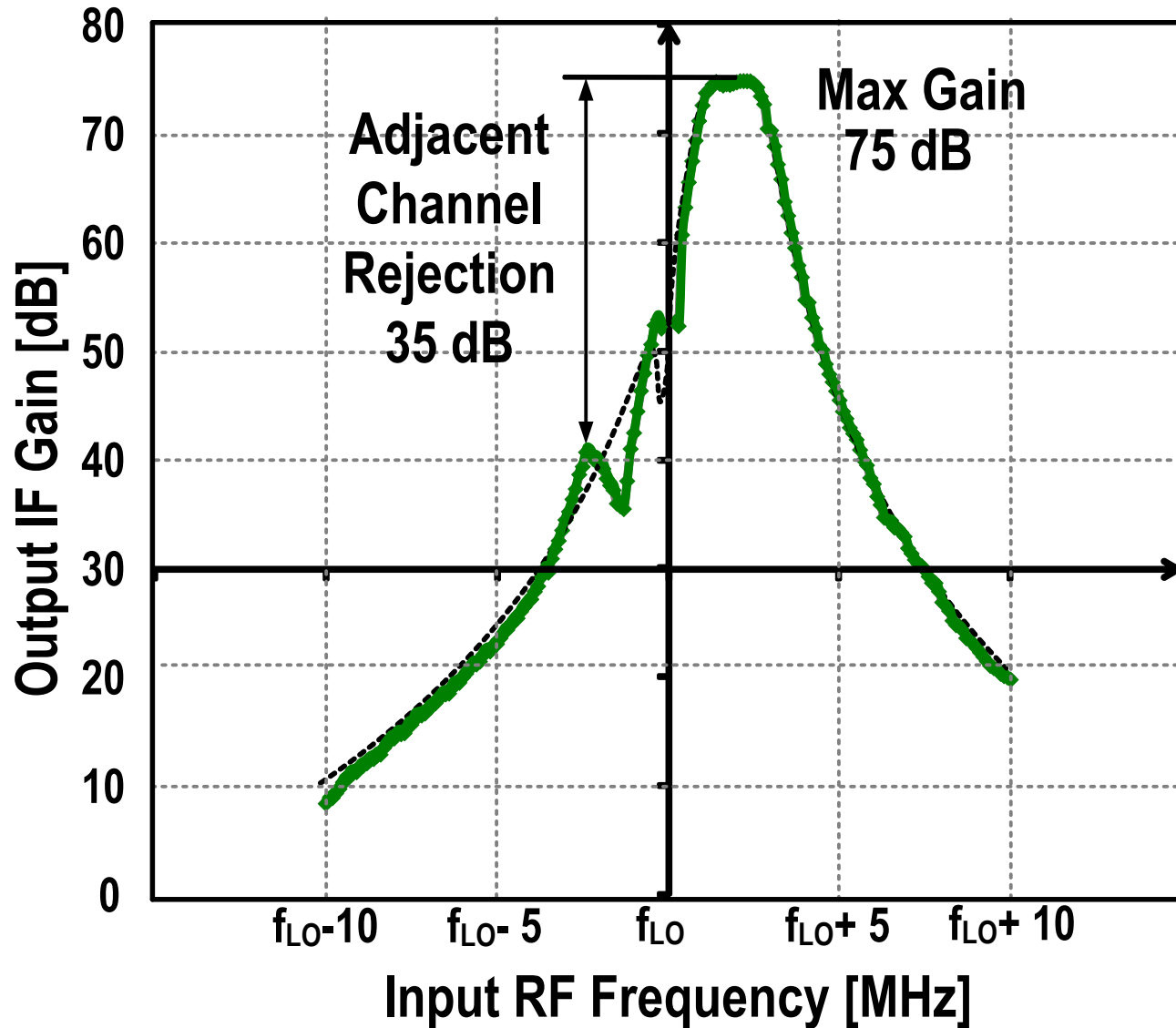

# Specs and State of Art

	[1]	[2]	This work
NF (dB)	24.7	5.7	9
Sensitivity (dBm)	-82	-101	-94.7
IIP3(dBm)	-4,5	-16	-12,5
SFDR (dB)	50.3	55.3	55.5
Image Rejection (dB)	---	36	35
PN(3.5MHz) (dBc/Hz)	--	--	-116
Vdd (V)	1.8	1.8	1.2
Power dissipation (mW)	15	17	3.6
Number of inductors	6	4	1
Area (mm <sup>2</sup> )	2.1	0.8	0.35
Technology (μm)	0.18	0.18	0.09

[1] *P. Choi, et al.*, JSSC, Dec 2003 (802.15.4)

[2] *W. Kluge, et al.*, JSSC, Dec. 2006 (ZigBee)

# Outline

---

- **The LNA-Mixer-VCO cell**
  - The LC tank Oscillator as a Mixer
  - Single/Double Switching Pair SOM
  - LNA introduction
- **Loss Mechanisms in the SOM**
  - Output parasitic capacitances
  - Common Mode and Differential losses
  - Voltage Mode vs. Current Mode
- **I & Q LMV Cells**
  - Quadrature at the VCO
  - Quadrature at the RF signal path
- **Prototypes**
  - GPS RF Front-End
  - ZigBee Receiver
- **Conclusions**

# Conclusions

---

- The functionalities of RF amplification, mixing and LO generator were successfully merged in a single stage.
- The LMV cell represents a competitive solution to reduce power consumption and area ,compatible with low voltage supply.
- The LMV cell was advantageously used in a very low power GPS quadrature front-end and a ZigBee receiver

# Acknowledgements

---

Thanks to:

Andrea Mazzanti, Marika Tedeschi, Riccardo Tonietto, Luca Vandi,  
Piero Andreani, and Rinaldo Castello